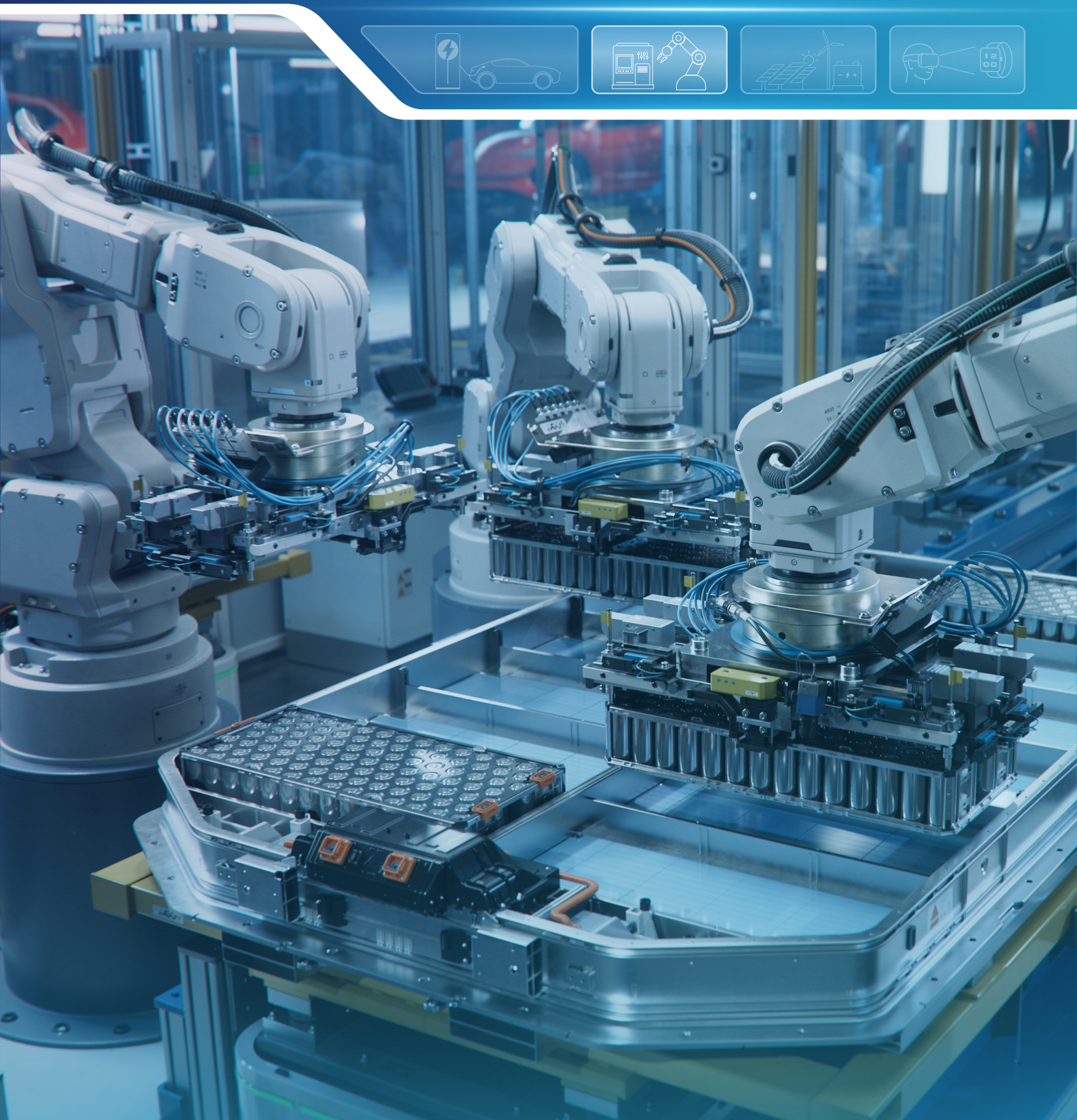


# How to Calculate the Threshold of NSI8608 Digital Input

AN-13-0007

Author: Runsheng Zhou, Huafu Mao



# How to Calculate the Threshold of NSI8608 Digital Input

## ABSTRACT

The NSI8608 is a multi-channel digital isolation chip that supports digital inputs specified in IEC 61131-2. The chip supports digital signal inputs up to 60v without the need for separate power supply on the input side and provides isolated digital outputs. The internal integrated rectifier bridge supports both source and drain inputs. The input also integrates a current limiting function to effectively reduce the overall temperature of the solution.

In system design, different system requirements have different requirements for the voltage transition threshold and current of the chip, which can be calculated from the peripheral resistance. The NSI8608 has a simpler peripheral design than similar products on the market. This note explains how to calculate the threshold of relevant parameters and gives an example of calculation.

## INDEX

<b>1. CHIP CHARACTERISTICS</b> .....	<b>2</b>
1.1.FUNCTIONAL BLOCK DIAGRAM .....	2
1.2.IV CHARACTERISTIC CURVE OF INPUT .....	2
1.3.INPUT THRESHOLD VOLTAGE .....	3
1.4.Input Current Limiting Function .....	4
<b>2. THRESHOLD CALCULATION</b> .....	<b>5</b>
2.1.NO NEED TO ADJUST CURRENT .....	5
2.2.NEED TO ADJUST CURRENT .....	6
2.3.APPLICATION EXAMPLE AND CALCULATION TOOL .....	6
<b>3. SYSTEM HEATING DESIGN</b> .....	<b>7</b>
3.1.CALCULATION OF CHIP POWER CONSUMPTION .....	7
3.2.MAXIMUM OPERATING AMBIENT TEMPERATURE OF CHIP .....	7
3.3.RELATIONSHIP BETWEEN CHIP POWER CONSUMPTION AND AMBIENT TEMPERATURE .....	8
3.4.HEATING MEASUREMENT .....	9
<b>4. REVISION HISTORY</b> .....	<b>10</b>

# How to Calculate the Threshold of NSI8608 Digital Input

## 1. Chip Characteristics

### 1.1. Functional Block Diagram

As shown in Figure 1.1, the chip input integrates a rectifier bridge to achieve positive and negative voltage inputs, and reduces chip power consumption through a current limiting module. The chip input first reaches the current limiting module through the internal rectifier bridge, and supplies power to other circuits at the same time.

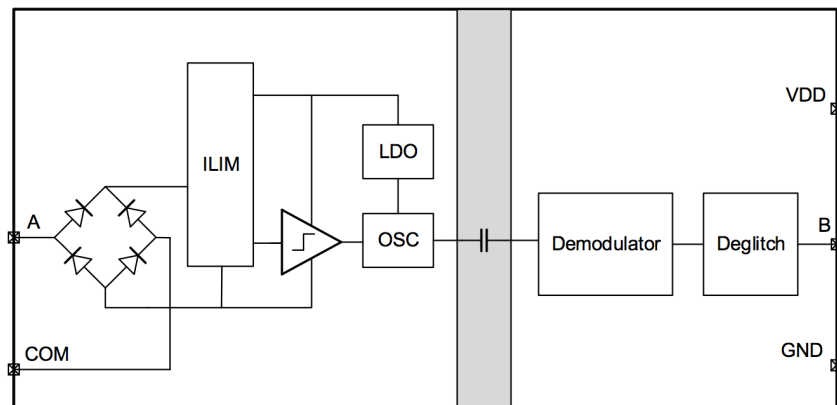


Figure 1.1 Functional Block Diagram

### 1.2. IV Characteristic Curve of Input

The relationship between input voltage and input current of the chip is shown in Figure 1.2. The voltage must first reach the forward conduction voltage of the diode, after which the current increases approximately linearly with the increase in voltage until the current hardly changes anymore after reaching the input current limit.

# How to Calculate the Threshold of NSI8608 Digital Input

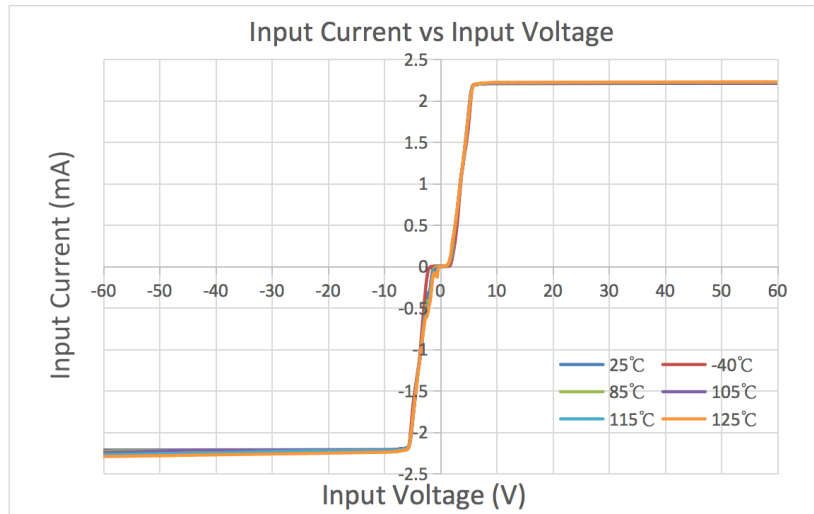


Figure 1.2 Relationship Between Input Current and Input Voltage

### 1.3. Input Threshold Voltage

The chip's input threshold voltage range is shown in the table below. It can work normally without a series threshold resistor ( $R_{THR}$ ). The relationship between the threshold voltage and temperature of the chip is shown in Figure 1.3.

Parameters	Symbol	Min	Typ	Max	Unit	Comments
High level threshold voltage	VIH		8	9.2	V	voltage at Ax
Low level threshold voltage	VIL	6.1	7.3		V	
Threshold voltage hysteresis	VHYS		0.7		V	

# How to Calculate the Threshold of NSI8608 Digital Input

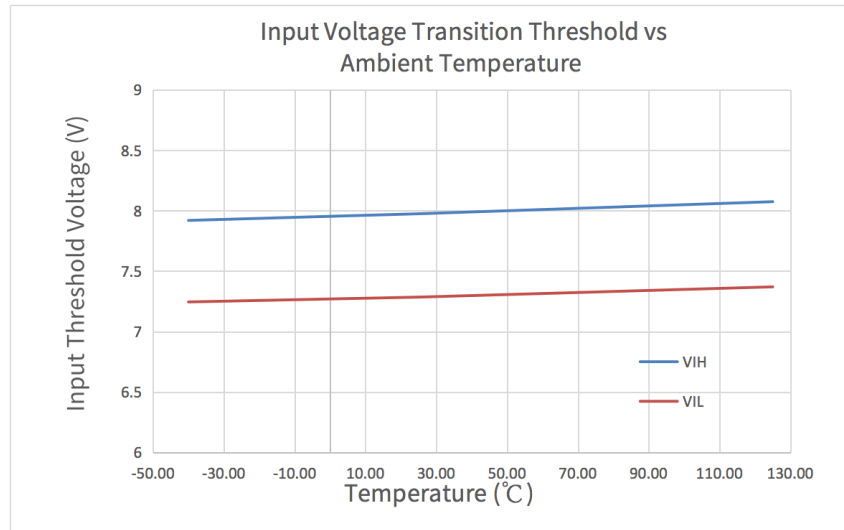


Figure 1.3 Relationship Between Threshold Voltage and Temperature

## 1.4. Input Current Limiting Function

The current limiting function integrated in the chip does not require a resistor for configuration. As long as the voltage reaches the voltage range, it can enter the current limiting state. The current limiting range is shown in the table below. Considering the overall heating of the system, the current is controlled in a very small range. If the system needs a larger current, the solution can be designed according to the method described below.

Parameters	Symbol	Min	Typ	Max	Unit	Comments
current drawn from Ax pin	IAx	1.55	2.1	2.62	mA	$V_{IL} \leq  V_{Ax}  \leq 60V$

# How to Calculate the Threshold of NSI8608 Digital Input

## 2.Threshold Calculation

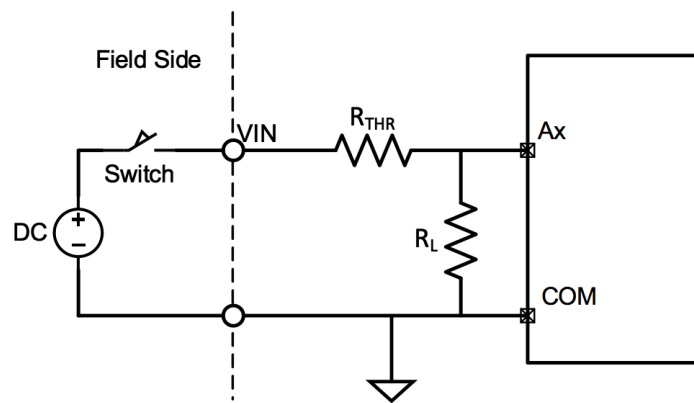


Figure 2.1 Input Peripheral Circuit

The device arrangement in the figure above is given for the chip input threshold design, which can be selected according to the instructions below.

First, you need to confirm whether the current limiting range of the chip itself can meet the system requirements. If it can, just refer to Section 2.1 to adjust the resistor  $R_{THR}$  to adapt to the voltage threshold requirements without the need to use the resistor  $R_L$ . If the system requires a larger current, refer to Section 2.2 to design the resistance values of  $R_{THR}$  and  $R_L$ .

### 2.1.No Need to Adjust Current

When the system does not need to adjust the current limit, there is no need to use the  $R_L$  resistor. The threshold can be calculated using the following formula:

- $V_{IN} = V_{Ax} + I_{Ax} * R_{THR}$

$V_{IN}$ : External input voltage requirement

$V_{Ax}$ : Voltage at chip pins

$I_{Ax}$ : Chip current limit

$R_{THR}$ : Series threshold resistance

Generally, the system has a clear requirement for the ON/OFF state voltage. At this time, the voltage value is substituted into  $V_{IN}$  and  $V_{Ax}$  is substituted into the chip  $V_{IH}/V_{IL}$  value to calculate the range of the threshold resistor  $R_{THR}$ . You can also directly use the Excel tool provided by NOVOSENSE for calculation.

# How to Calculate the Threshold of NSI8608 Digital Input

## 2.2. Need to Adjust Current

When the system requires a larger current IIN, both RTHR and RL need to be used to meet the requirement. The specific formula is as follows:

$$IIN = IAX + VAX / RL \quad \text{---(1)}$$

$$VIN = (IAX + VAX / RL) * RTHR + VAX \quad \text{---(2)}$$

IIN: External input current requirement

VIN: External input voltage requirement

VAX: Voltage at chip pins

IAX: Chip current limit

RTHR: Series threshold resistance

RL: Shunt bleed resistance

There is a contradictory relationship between the shunt bleed resistance and the series threshold resistance, that is, the greater the bleed, the greater the series resistance voltage drop. Therefore, it is necessary to first calculate the maximum value of RL by formula (1), and then calculate the maximum value of RTHR.

## 2.3. Application Example and Calculation Tool

Suppose that the existing system requires an ON state at an input voltage of up to 15V and the current must be at least 3mA at this time. The following explains how to design using the above method.

- 1) First determine whether the chip can meet the current requirement of the ON state. Obviously, the minimum requirement of 3mA exceeds the maximum value of chip IAX. At this time, the current needs to be adjusted using the peripheral design method in Section 2.2.
- 2) Substitute the minimum current requirement and maximum voltage requirement into formula (1) or the calculation tool to calculate the maximum value of RL. The maximum value calculated at this time is 6.34kohm.
- 3) Select the maximum value of RL obtained in the previous step, for example, 5kohm, and substitute this value into formula (2) or the calculation tool to obtain the maximum value of RTHR.

RTHR(kohm)	RL(kohm)	I <sub>lim</sub> (mA)	min	typ	max
0	\	VIL(V)	6.10	7.30	
		VIH(V)		8.00	9.20
Maximum recommended resistance		customer specification input			
1.30	6.34	VIN(V)	15		
		IIN(mA)	3		
		RL	5		

The maximum RL value is calculated on the left side after filling in the VIN and IIN. Select the appropriate RL resistance value and fill it in here. The RTHR maximum value will be calculated on the left side.

Figure 2.2 Demonstration of Calculation Tool

# How to Calculate the Threshold of NSI8608 Digital Input

## 3. System Heating Design

System heating is an important part of system design. The following compares the NSI8608 and its peripheral design with other solutions, illustrates the advantages of the NSI8608 solution, and provides technical suggestions related to heating. In the discrete optocoupler solution, it is difficult to achieve multi-channel integration due to the characteristics of the optocoupler device itself. Although heating is relatively easy to control, the overall solution is costly and requires a large PCB footprint, making it only suitable for individual applications with a small number of channels.

Another common solution is the multi-channel integrated capacitive isolation DI. Although it solves the large PCB footprint problem of the discrete solution, the lack of integrated current limiting function causes serious heating around the peripheral devices and chip, forcing the increase of the spacing with other systems and the increase of the heat dissipation area to reduce the overall system temperature.

The NSI8608 effectively controls system heating from two dimensions: heating of the chip itself and heating of the peripheral devices, reducing the PCB footprint and also the selection pressure and cost of the peripheral devices.

### 3.1. Calculation of Chip Power Consumption

Due to the integrated current limiting function inside the chip, the power consumption calculation of the NSI8608 itself is very simple. The specific formula is as follows:

- $W = \sum V_{Ax} * I_{Ax} * \eta$

W: Total power consumption of the chip

V<sub>Ax</sub>: Voltage at chip pins

I<sub>Ax</sub>: Chip current limit

η: Signal duty cycle

x: Channel number actually used

Specifically, I<sub>Ax</sub> can be directly based on the current limiting range in the chip manual, and the voltage of V<sub>Ax</sub> can be calculated based on threshold calculation in the previous section.

### 3.2. Maximum Operating Ambient Temperature of Chip

To calculate the maximum operating ambient temperature of the chip, you need to confirm the corresponding thermal resistance first. The following table shows the thermal resistance of the two packages of NSI8608.



## How to Calculate the Threshold of NSI8608 Digital Input

Parameters	Symbol	SSOP16	SSOP20	Unit
Junction-to-ambient thermal resistance	$\theta_{JA}$	86.3	67.1	$^{\circ}\text{C}/\text{W}$

The chip power  $W$  under different application conditions is calculated according to the chip power consumption calculation formula, and the maximum junction temperature of the chip  $T_{jmax} = 150^{\circ}\text{C}$

Maximum operating ambient temperature of chip:  $T_{max} = T_{jmax} - W * \theta_{JA}$

### 3.3. Relationship Between Chip Power Consumption and Ambient Temperature

Based on the chip power consumption calculation formula, the maximum power consumption of the NSI8608 chip can be calculated as  $W_{max} = 1257.6 \text{ mW}$  ( $60\text{V} * 2.62\text{mA} * 8$ ), the corresponding package thermal resistance is  $67.1^{\circ}\text{C}/\text{W}$ , and the maximum ambient temperature is calculated as  $T_{max} = 65.6^{\circ}\text{C}$  ( $150^{\circ}\text{C} - 1257.6 \text{ mW} * 67.1^{\circ}\text{C}/\text{W}$ ).

Based on the above parameters, the relationship between power consumption and operating temperature under extreme conditions of the chip is shown in the figure below.

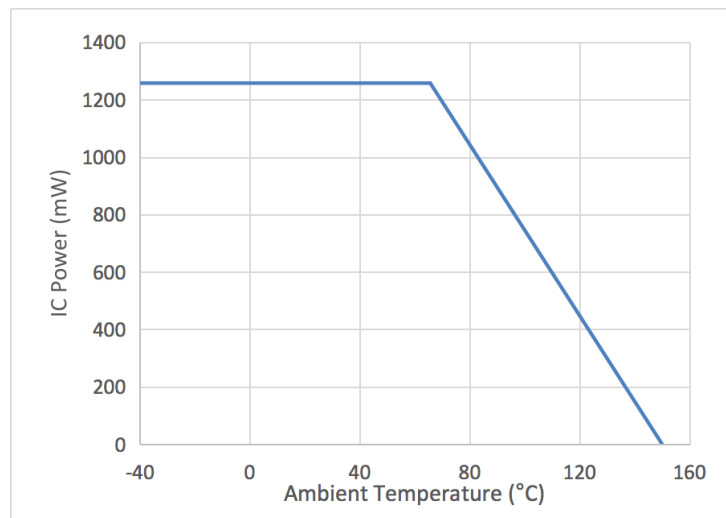


Figure 3.1 Relationship between Ambient Temperature and Chip Power Consumption

# How to Calculate the Threshold of NSI8608 Digital Input

## 3.4. Heating Measurement

Under room temperature of 25°C, the peripheral circuit is set up according to IEC 61131-2 type-3 ( $R_{THR}=0\Omega$ ,  $R_i$  is not used), and the heating test of single-channel 30V DC input is as shown in the figure below (tested using NOVOSENSE's DEMO board, front view in the left picture and back view in the right picture).

The NSI8608 integrates a current limiting design, which effectively controls both global and local heating.

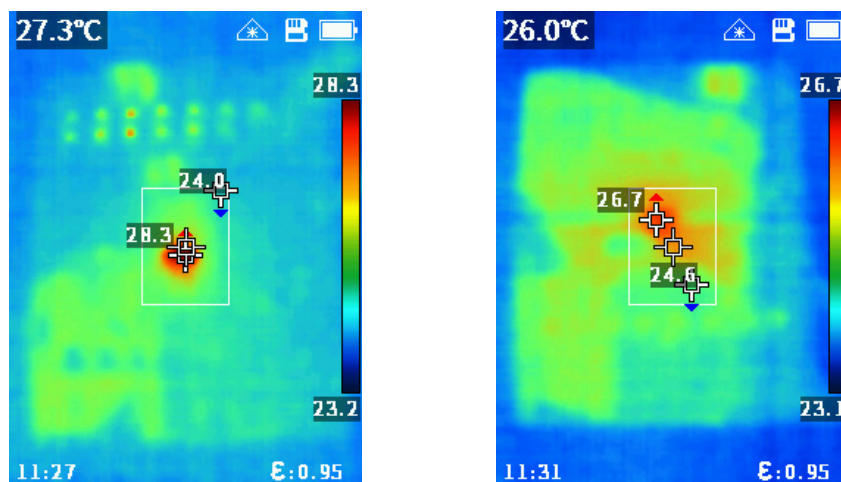


Figure 3.2 Infrared Thermal Imaging of NSI8608 in Operation

# How to Calculate the Threshold of NSI8608 Digital Input

## 4.Revision History

Revision	Description	Author	Date
1.0	Initial version	Runsheng Zhou, HuaFu Mao	10/9/2024

Sales Contact: [sales@novosns.com](mailto:sales@novosns.com); Further Information: [www.novosns.com](http://www.novosns.com)

### IMPORTANT NOTICE

The information given in this document (the “Document”) shall in no event be regarded as any warranty or authorization of, express or implied, including but not limited to accuracy, completeness, merchantability, fitness for a particular purpose or infringement of any third party’s intellectual property rights.

Users of this Document shall be solely responsible for the use of NOVOSENSE’s products and applications, and for the safety thereof. Users shall comply with all laws, regulations and requirements related to NOVOSENSE’s products and applications, although information or support related to any application may still be provided by NOVOSENSE.

This Document is provided on an “AS IS” basis, and is intended only for skilled developers designing with NOVOSENSE’ products. NOVOSENSE reserves the rights to make corrections, modifications, enhancements, improvements or other changes to the products and services provided without notice. NOVOSENSE authorizes users to use this Document exclusively for the development of relevant applications or systems designed to integrate NOVOSENSE’s products. No license to any intellectual property rights of NOVOSENSE is granted by implication or otherwise. Using this Document for any other purpose, or any unauthorized reproduction or display of this Document is strictly prohibited. In no event shall NOVOSENSE be liable for any claims, damages, costs, losses or liabilities arising out of or in connection with this Document or the use of this Document.

For further information on applications, products and technologies, please contact NOVOSENSE ([www.novosns.com](http://www.novosns.com)).

**Suzhou NOVOSENSE Microelectronics Co., Ltd**